

Kirchhoff's Voltage Law (KVL)



KVL

The sum of all the voltage drops around a single closed path in a circuit is equal to the total source voltage in that loop.

$$V_S = V_1 + V_2 + V_3 + \dots + V_n$$

► FIGURE 30

Illustration of voltage polarities in a closed-loop circuit.

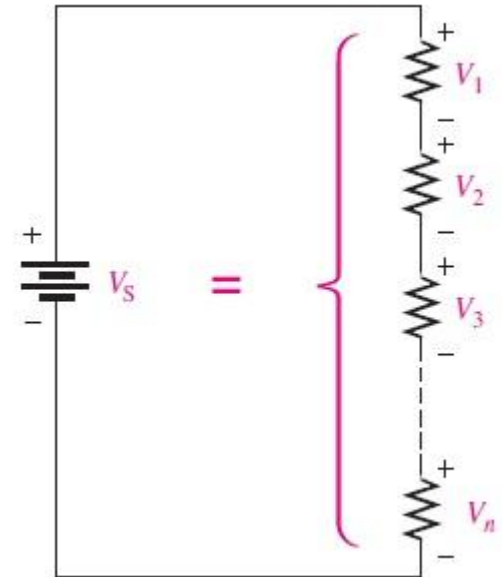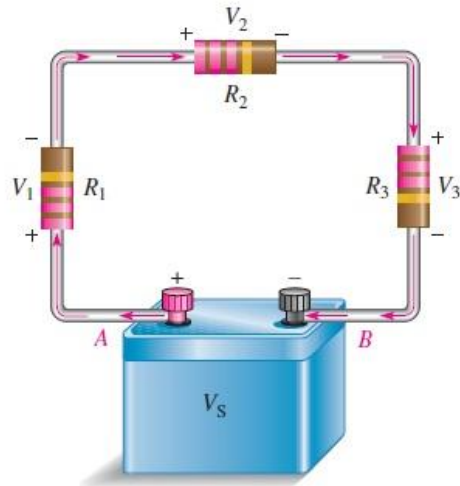

KVL Cont...

The algebraic sum of all the voltages (both source and drops) around a single closed path is zero.


Therefore, another way of expressing Kirchhoff's voltage law in equation form is

$$V_S - V_1 - V_2 - V_3 - \dots - V_n = 0$$

EXAMPLE 13

Determine the source voltage V_S in Figure 33 where the two voltage drops are given. There is no voltage drop across the fuse.


► FIGURE 33

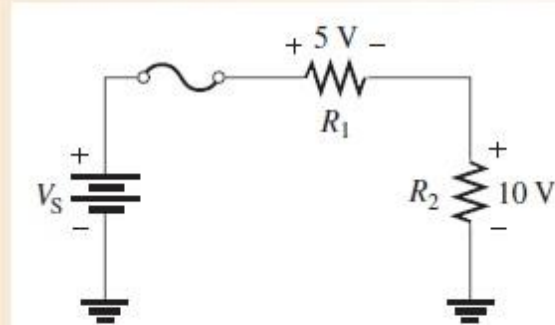

EXAMPLE 14

Find the value of R_4 in Figure 34.

► FIGURE 34

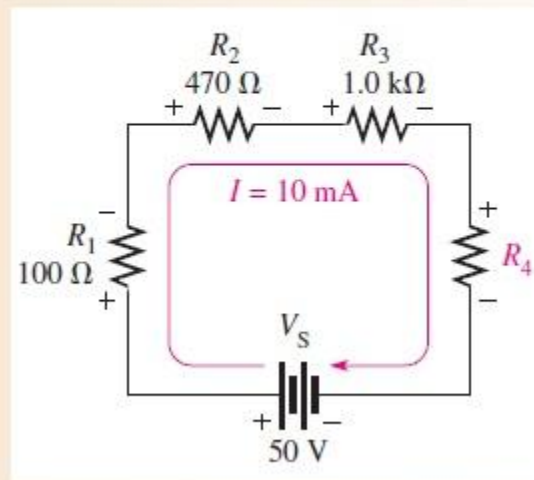

Determine the unknown voltage drop, V_3 , in Figure 35.

► FIGURE 35

