

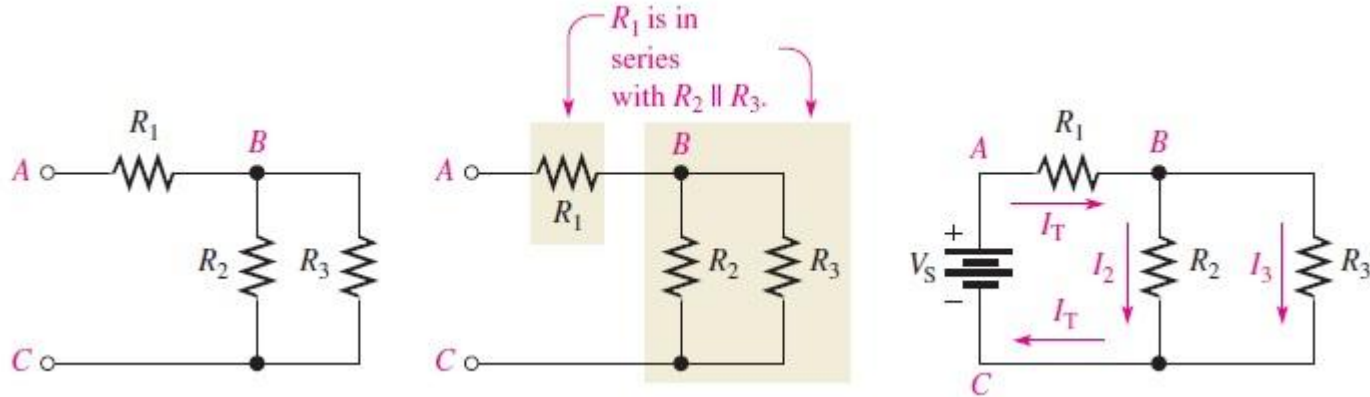
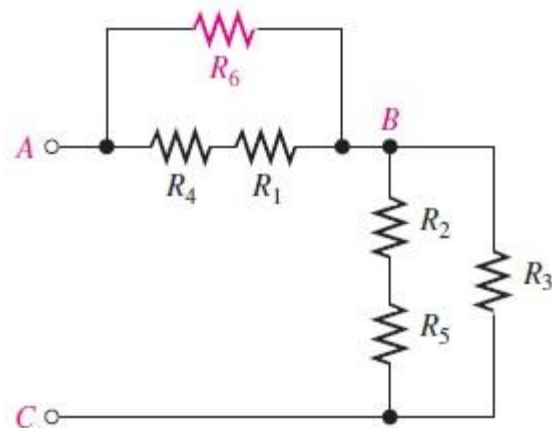


Series-Parallel Resistive Circuits


IDENTIFYING SERIES-PARALLEL RELATIONSHIPS

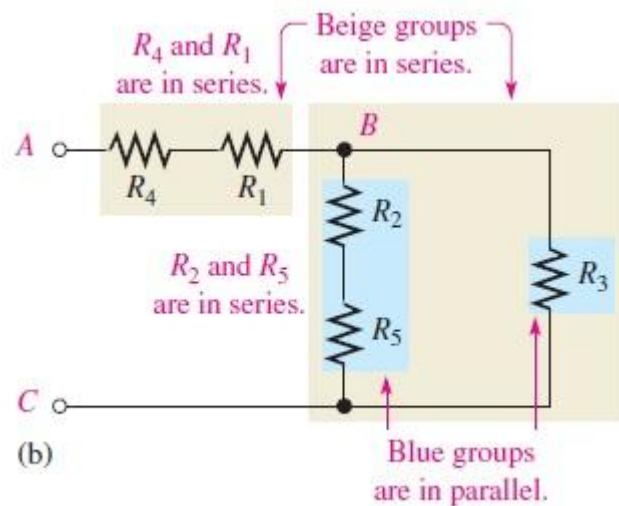
A series-parallel circuit consists of combinations of both series and parallel current paths. It is important to be able to identify how the components in a circuit are arranged in terms of their series and parallel relationships.



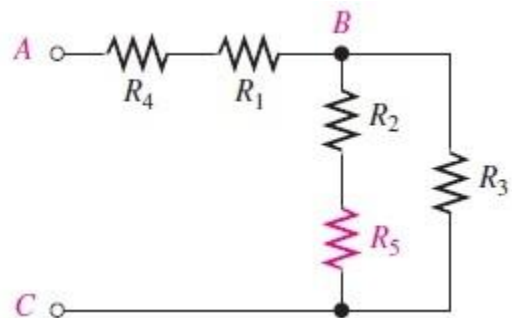


(a)

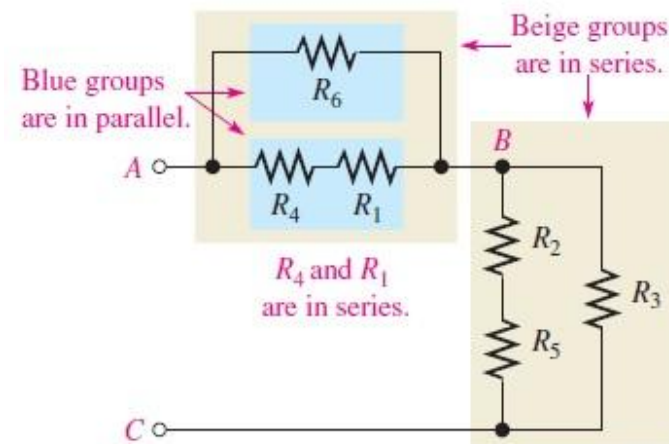


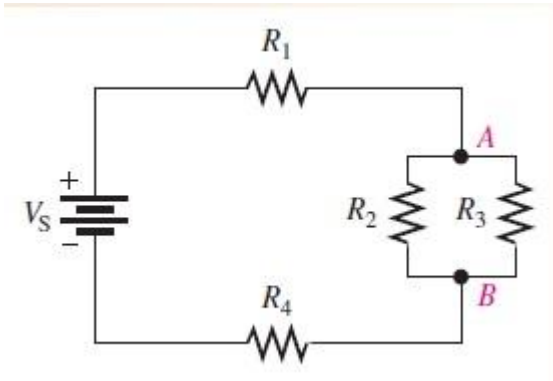


Solution in Class

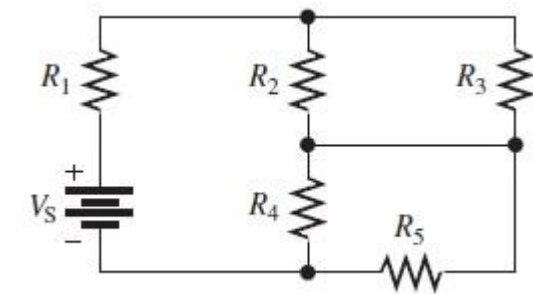





Solution in Class

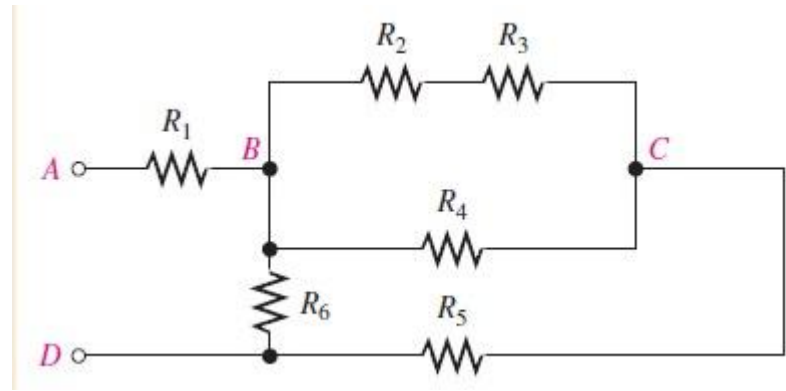

Solution in Class

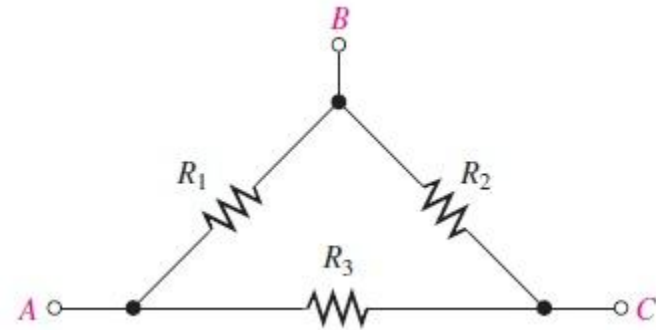

Solution in Class

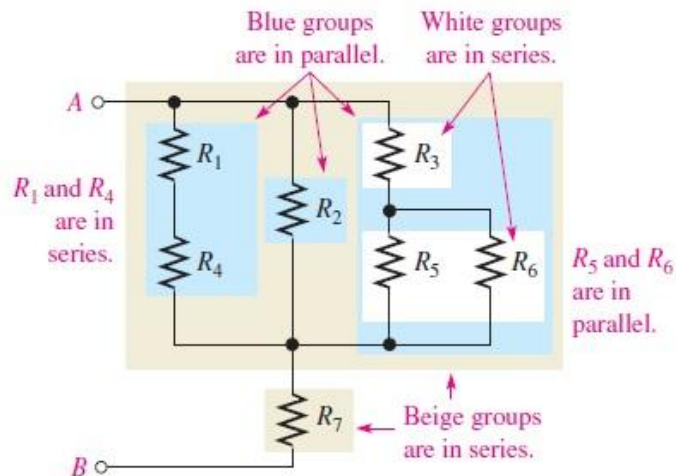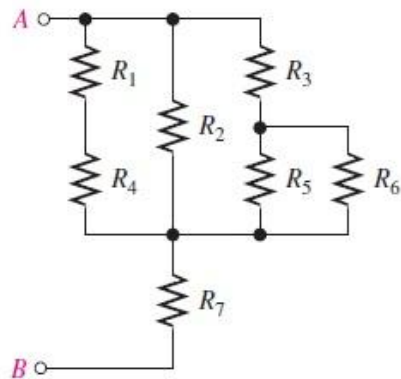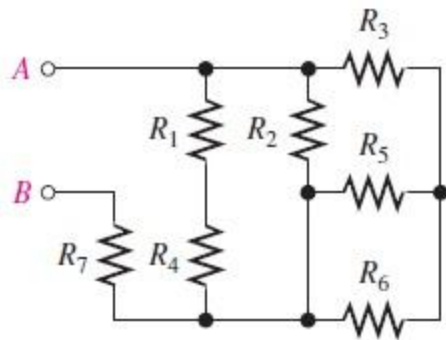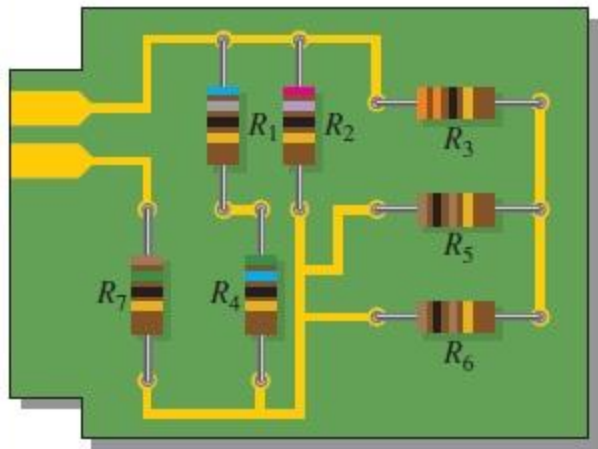

ANALYSIS OF SERIES-PARALLEL RESISTIVE CIRCUITS

Analyze series-parallel circuits


- ◆ Determine total resistance
- ◆ Determine all the currents
- ◆ Determine all the voltage drops

Total Resistance


To find the total resistance () of a series-parallel combination, simply define the series and parallel relationships; then perform the calculations that you have previously learned.

Determine R_T of the circuit in Figure 16 between terminals A and B.

► FIGURE 16

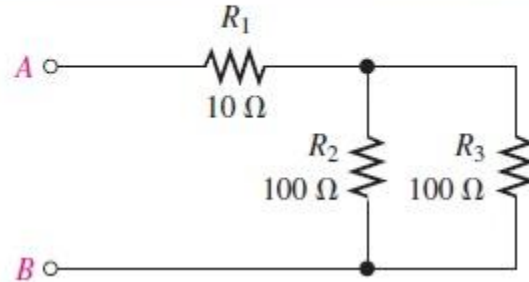

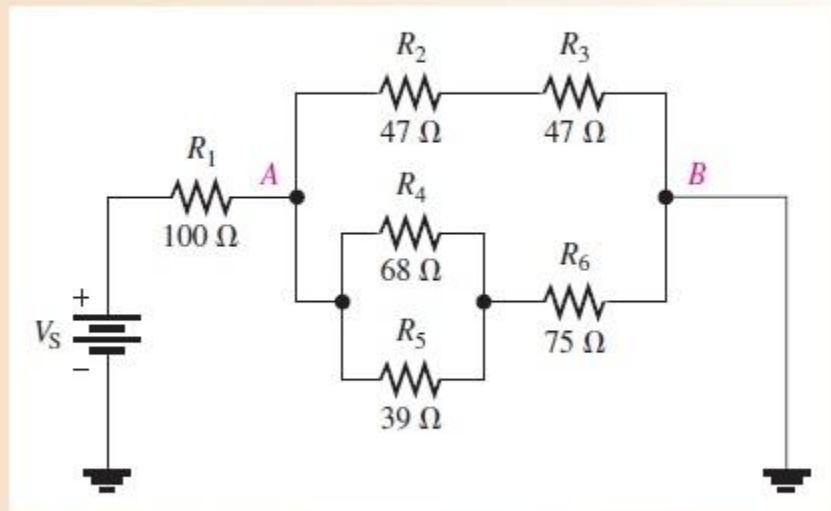Find the total resistance between the positive and negative terminals of the battery in Figure 17.



▲ FIGURE 17

Total Current


Once you know the total resistance and the source voltage, you can apply Ohm's law to find the total current in a circuit. Total current is the source voltage divided by the total resistance.

$$I_T = \frac{V_S}{R_T}$$

Branch Currents

Using the current-divider formula, Kirchhoff's current law, Ohm's law, or combinations of these, you can find the current in any branch of a series-parallel circuit. In some cases, it may take repeated application of the formula to find a given current.

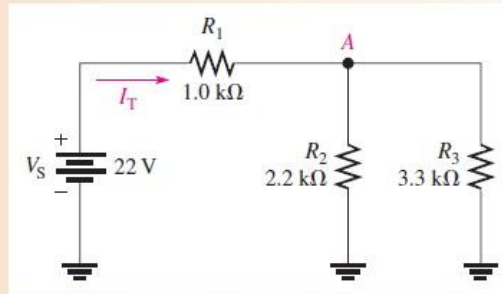Find the current through R_2 and the current through R_3 in Figure 19.



▲ FIGURE 19


Voltage Drops

To find the voltages across certain parts of a series-parallel circuit, you can use the voltage divider formula, Kirchhoff's voltage law, Ohm's law, or combinations of each.

EXAMPLE 10


Determine the voltage drop from node A to ground in Figure 21. Then find the voltage (V_1) across R_1 .

► FIGURE 21

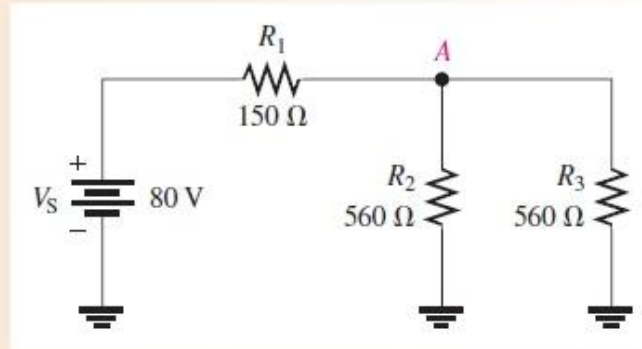

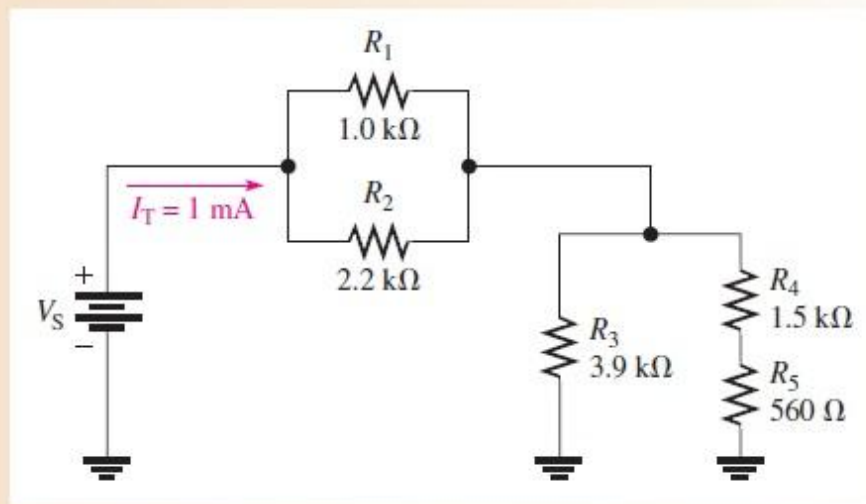EXAMPLE 11

Determine the voltage drop across each resistor in the circuit of Figure 23.



▲ FIGURE 23